

- 7.1 Assuming the diode is conducting the current is found to be

$$I = \frac{V_E - V_D}{5 + 10} = -\frac{2}{15} = -0.133 \text{ A}$$

The voltage across the diode is

$$\begin{aligned} V_D &= (-10I + V_E) - (-5I + V_D) \\ &= -1.33 + 10 - 0.667 - 12 = -3.997 \text{ V} \end{aligned}$$

This result contradicts the assumption, since the diode cannot conduct if V_D is negative.

Thus, the diode must be off.


7.4 a) $R = \frac{5 - 0.7}{5 \times 10^{-3}} = 860 \Omega$

b) $I = \frac{E_{\text{min}} - 0.7}{860} = 1 \times 10^{-3}$

$$\Rightarrow E_{\text{min}} = 0.86 + 0.7 = 1.56 \text{ V}$$

- 7.6
- a) RB
 - b) FB
 - c) RB
 - d) FB
 - e) FB

7.7

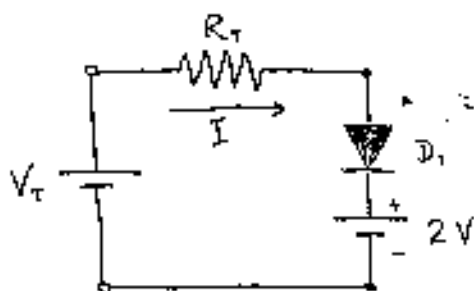

The Thévenin equivalent resistance is

$$R_T = 500 \parallel 1000 = \frac{1000}{3} \Omega$$

The Thévenin equivalent voltage is

$$V_T = \frac{V_{in}}{1500} \times 1000 = \frac{2}{3} \times V_{in}$$

The current I is

$$I = \frac{V_T - 2}{R_T} = \frac{\frac{2}{3} \times V_{in} - 2}{\frac{1000}{3}} = \frac{V_{in} - 3}{500}$$

To keep diode D_1 FB, the current I , must be greater than or equal zero.

Therefore, the range of V_{in} is

$$V_{in} \geq 3V$$

- 7.8 If diode D_2 is conducting, the voltage at the node to the left of D_1 will be 5V and D_1 will conduct. To ensure that D_2 is conducting, voltage V_{in} must be greater than 5V.

Assume D_2 is cut off. D_1 will conduct as long as V_{in} is greater than zero. Thus, the value for D_1 to conduct is

$$V_{in} > 0$$

- 7.9 a) D_2 and D_4 are FB ; D_1 and D_3 are RB .

$$V_{out} = -5 + 0.7 = -4.3 \text{ V}$$

- b) D_1 and D_2 are RB ; D_3 is FB .

$$V_{out} = -10 + 0.7 = -9.3 \text{ V}$$

- c) D_1 is RB ; D_2 is FB .

$$V_{out} = 5 - 0.7 = 4.3 \text{ V}$$

- 7.11 Assume D_1 is conducting ; the diode current is

$$I = \frac{V_{in} - 2}{1500} = \frac{6}{1500} = 4 \text{ mA}$$

Since the current is positive, the initial assumption was correct.

The output voltage V_o is

$$V_o = 500 I + 2 = 4 \text{ V}$$

7.15 a) The voltage across the diode is

$$V_z = V_s \left(\frac{50 + 50}{100 + 50 + 50} \right) = 6 < 7.7 \text{ V}$$

Therefore, the Zener diode is off. Thus, the output voltage is:

$$V_{out} = 6 \left(\frac{50}{100} \right) = 3 \text{ V}$$


b) The voltage across the diode is

$$V_z = 20 \left(\frac{100}{200} \right) = 10 > 7.7 \text{ V}$$


In this case, the Zener diode is on and the output voltage is:

$$V_{out} = 7.7 \left(\frac{50}{100} \right) = 3.85 \text{ V}$$


7.24

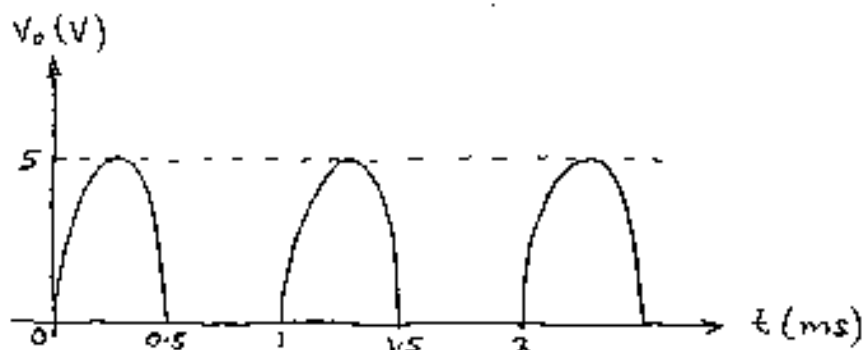

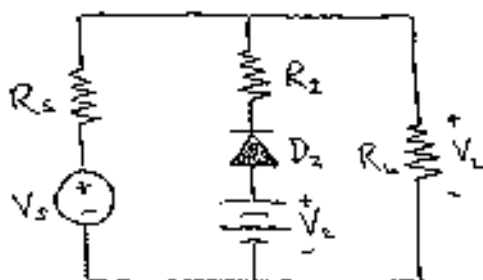7.36 For $0 < V_s < V_2 = 12V$, the circuit is shown below.



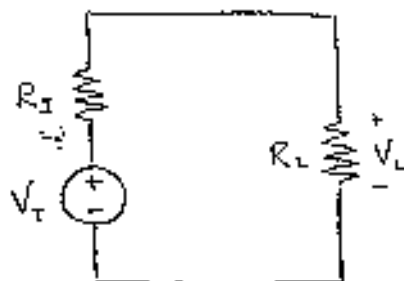The Thevenin equivalent circuit is the following:



where,

$$V_T = \frac{V_s - V_2}{R_s + R_2} \times R_2 + V_2$$

$$= \frac{1}{3} V_s + 8V$$

$$R_T = \frac{5 \times 10}{15} = \frac{10}{3} \Omega$$


Thus, the load voltage is given by the expression

$$V_L = \frac{R_L}{R_L + R_T} \times V_T = 0.3125 V_s + 7.5V$$

For $12 < V_s < 15$, V_L is given by

$$V_L = \frac{5}{6} V_s = 0.833 V_s$$

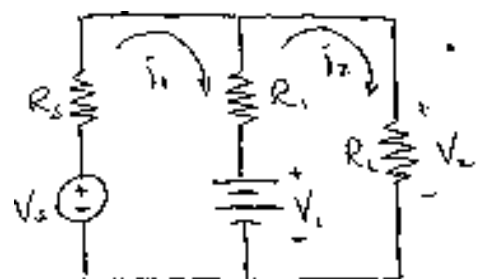For $15 < V_s < 20$, the equivalent circuit is shown below.



Applying mesh analysis,

$$i_1(R_s + R_1) - i_2 R_1 = V_s - V_1$$


$$i_2(R_1 + R_L) - i_1 R_1 = V_1$$

We find that

$$V_L = R_L \times i_2 = R_L \times \frac{V_s + 15}{110}$$

$$= 0.4545 V_s + 6.818$$

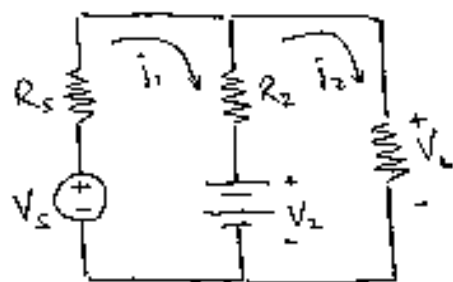For $-20 < V_s < 0$, the circuit is the following:



and

$$i_1(R_s + R_2) - i_2 R_2 = -V_2 + V_s$$


$$i_2(R_2 + R_L) - i_1 R_2 = V_2$$

so that

$$V_L = i_2 \times R_L = \frac{24 + V_s}{160} \times 50$$

$$= 7.5 + 0.3125 V_s$$

The $V_L - V_s$ characteristic:

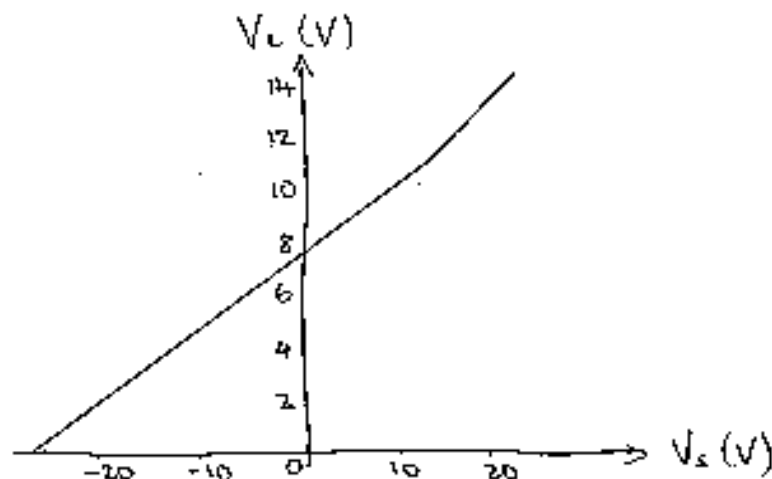

7.39 For fig. P7.36 (a):

a) At $t = t_i^-$, before the switch S_1 closes, we have

$$\begin{aligned} I_{sw} &= 0 \\ I_s &= I_B = \frac{V_s - V_{\text{battery}}}{R_s + R_B} \\ &= \frac{13 - 9.6}{11} = 0.31 \text{ A} \end{aligned}$$

b) At $t = t_i^+$, we have

$$\begin{aligned} \therefore I_s &= 13 \text{ A}, \quad I_B = -0.96 \text{ A} \\ I_{sw} &= I_s - I_B = 13.96 \text{ A} \end{aligned}$$

c) The battery voltage will drop quickly because of the small resistance in the circuit.

For fig. 7.36 (b):

a) At $t = t_i^-$, we have

$$\begin{aligned} I_{sw} &= 0 \\ I_s &= I_B = \frac{V_s - V_{\text{battery}} - V_D}{R_s + R_B} \\ &= \frac{13 - 9.6 - 0.6}{11} = 0.25 \text{ A} \end{aligned}$$

b) At $t = t_i^+$, we have

$$I_s = I_{sw} = 13 \text{ A}, \quad I_B = 0$$

c) The battery will not be drained, because of the large reverse resistance of the diode.