
8.1

(a) Since $V_{BE} = 0.8$ V, the BE junction is forward biased.

$$\begin{aligned}V_{CB} &= V_{CE} + V_{EB} \\ &= 0.4 + (-0.8) = -0.4 \text{ V}\end{aligned}$$

Thus, the CB junction is forward biased.

Therefore, the transistor is in the saturation region.

(b)

$$\begin{aligned}V_{BE} &= V_{BC} + V_{CE} \\ &= -1.4 + 2.1 = 0.7 \text{ V}\end{aligned}$$

The EB junction is forward biased.

$V_{CB} = 1.4$ V, the CB junction is reverse biased.

Therefore, the transistor is in the active region.

(c) $V_{CB} = 0.9$ V for a pnp transistor implies that the CB junction is forward biased.

$$\begin{aligned}V_{BE} &= V_{BC} - V_{CE} \\ &= -0.9 - 0.4 = -1.3 \text{ V}\end{aligned}$$

The BE junction is forward biased.

Therefore, the transistor is in the saturation region.

(d) With $V_{BE} = -1.2$ V, the BE junction is reverse biased. $V_{CB} = 0.6$: the CB junction is reverse biased. Therefore, the transistor is in the cut-off region.

8.3

$$(a) I_E = I_C + I_B = 1 \text{ mA} + 20 \mu\text{A} = 1.02 \text{ mA}$$

$$V_E = 1000 I_E = 1.02 \text{ V}$$

$$V_{RC} = 5000 I_C = 5 \text{ V}$$

$$V_{CB} = 20 - V_{RC} - V_{BE} - V_E \\ = 20 - 5 - 0.7 - 1.02 = 13.28 \text{ V}$$

The CB junction is reverse-biased.

Therefore, the transistor is operating in the active region.

$$(b) I_E = 3.2 \text{ mA} + 0.3 \text{ mA} = 3.5 \text{ mA}$$

$$V_E = 3.5 \text{ V}$$

$$V_{RC} = 16 \text{ V}$$

$$V_{CB} = 20 - 16 - 0.8 - 3.5 = -30 \text{ mV}$$

The CB junction is forward-biased.

Therefore, the transistor is operating in the saturation region.

$$(c) I_E = 3 \text{ mA} + 1.5 \text{ mA} = 4.5 \text{ mA}$$

$$V_E = 4.5 \text{ V}$$

$$V_{RC} = 22.5 \text{ V}$$

$$V_{CB} = 20 - 22.5 - 0.85 - 4.5 = -7.85 \text{ V}$$

The CB junction is forward-biased.

Therefore, the transistor is operating in the saturation region.

8.4

(a) In the pnp transistor, $V_{BE} = -0.6 \text{ V}$; the EB junction is forward biased.

$$V_{CB} = V_{CE} - V_{BE} \\ = -4 + 0.6 = -3.4 \text{ V}$$

The CB junction is reverse biased.

Therefore, the transistor is in the active region.

(b) For the npn transistor, $V_{CB} = 0.7 \text{ V}$; the CB junction is reverse biased.

$$V_{BE} = V_{BC} + V_{CE} \\ = -0.7 + 0.2 = -0.5 \text{ V}$$

The BE junction is reverse biased.

Therefore, the transistor is in cut-off region.

(c) For the npn transistor, $V_{BE} = 0.7 \text{ V}$; the BE junction is forward biased.

$$V_{BC} = V_{BE} - V_{CE} = 0.7 - 0.3 = 0.4 \text{ V}$$

The CB junction is forward biased.

Therefore, the transistor is in the saturation region.

(d) In the pnp transistor, $V_{CB} = -0.6 \text{ V}$; the CB junction is reverse biased.

$$V_{BE} = V_{BC} + V_{CE} \\ = 0.6 - 5.4 = -4.8 \text{ V}$$

The EB junction is forward biased.

Therefore, the transistor is in the active region.

8.5

$V_{BE} = 0.6V$ and the BE junction is forward biased.

$$I_B = \frac{V_{CC} - V_{BE}}{R_1} = \frac{12 - 0.6}{820k} = 13.9 \mu A$$

$$I_C = \beta I_B = 1.39 mA$$

Writing KVL around the right-hand side of the circuit:

$$-V_{CC} + I_C R_C + V_{CE} + I_B R_B = 0$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C - (I_B + I_C) R_B \\ &= 12 - (1.39 mA)(2.2 k\Omega) - (1.39 + 0.0139) mA(910\Omega) \\ &= 7.664V \end{aligned}$$

$$V_{BC} = V_{BE} + V_{CE} = 0.6 + 7.664 = 8.264V$$

$$V_{CB} > V_{BE} \Rightarrow \text{active region}$$

8.16

(a) From KVL:

$$-30 + I_{B1}(750k\Omega) + V_{BE1} = 0$$

$$I_{B1} = \frac{30 - 0.7}{750k} = 39.07 \mu A$$

$$I_{C1} = \beta I_{B1} = 3.907 mA$$

$$V_{C1} = 30 - (3.907 mA)(6.2 k\Omega) = 5.779V$$

$$V_{CE1} = V_{C1} = 5.779V$$

(b) Again, from KVL:

$$-5.779 + V_{BE2} + I_{B2}(4.7k\Omega) = 0$$

$$I_{B2} = \frac{5.779 - 0.7}{4.7k} = 1.081 mA$$

$$I_{C2} = I_{B2} \left(\frac{\beta}{\beta + 1} \right) = 1.081 mA \left(\frac{100}{101} \right) = 1.07 mA$$

Also,

$$-30 + I_{C2}(20k + 4.7k) + V_{CE2} = 0$$

$$V_{CE2} = 30 - (1.07 mA)(20k + 4.7k) = 3.574V$$

And,

$$I_{C2} = \frac{30 - V_{CE2}}{20k}$$

$$\Rightarrow V_{CE2} = 30 - (1.07 mA)(20k) = 8.603V$$

8.9

Applying KVL to the right-hand side of the circuit,

$$-V_{CC} + I_B R_B + V_{BE} = 0$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{20 - 0.6}{39k} = 497.4 \mu A$$

Since $\beta \gg 1$, $I_C \approx I_E = 497.4 \mu A$

Applying KVL to the left-hand side:

$$V_{CB} + I_C R_C - V_{DD} = 0$$

$$\begin{aligned} V_{CB} &= V_{DD} - I_C R_C \\ &= 20V - (497.4 \mu A)(20k\Omega) \\ &= 10.05V \end{aligned}$$

8.20

Assume $V_{CEsat} = 0.2V$, the current I_C can be found as

$$I_C \approx \frac{V_{CC} - V_{CEsat}}{R_C} = 4.8 mA$$

Therefore, $I_B = \frac{I_C}{\beta} = 0.096 mA = 96 \mu A$

Assuming $V_{\gamma} = V_{BEsat} = 0.6V$, we have

$$V_{BB} = I_B R_B + V_{BEsat} = 1.56V$$

That is $V_{BB} > 1.56V$