

9.7

$$(a) V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 6.03 \text{ V}$$

$$R_{BB} = R_1 \parallel R_2 = 1158.35 \Omega$$

Applying KVL around the base-emitter loop:

$$V_{BB} = I_B R_{BB} + V_{BE} + I_E R_E$$

Substituting for I_B ,

$$I_B = \frac{I_E}{\beta + 1}$$

We have

$$I_E = \frac{V_{BB} - V_{BE}}{R_E + R_{BB}/(\beta + 1)} = 48 \text{ mA}$$

The base current is:

$$I_B = \frac{I_E}{\beta + 1} = \frac{I_E}{101} = 0.475 \text{ mA}$$

The base voltage is

$$V_B = V_{BE} + I_E R_E =$$

$$= 0.6 + 48 \times 10^{-3} \times 100 = 5.4 \text{ V}$$

Assuming active-mode operation, the collector current is

$$I_C = \beta I_B = 47.5 \text{ mA}$$


The collector voltage can now be determined to be

$$V_C = 10 - 47.5 \times 10^{-3} \times 100 = 5.25 \text{ V}$$

Also

$$V_{CE} = V_C - V_E = 5.25 - 4.8 = 0.45 \text{ V}$$

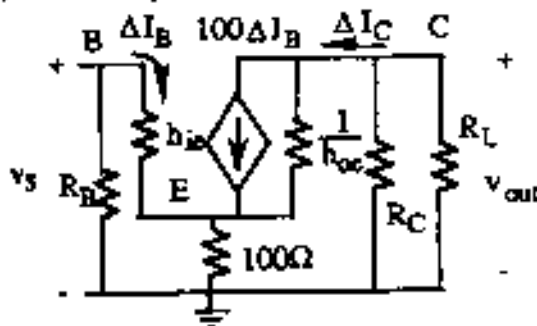b) The AC equivalent circuit is shown below



$$(c) h_{re} = \left. \frac{\partial v_{be}}{\partial v_{ce}} \right|_{I_B} \approx \frac{0.6}{0.475 \times 10^3} = 1.26 \text{ k}\Omega$$

$$R_B = R_1 \parallel R_2 = 1158.35 \Omega$$

$$R_C \parallel R_L = 60 \Omega$$

Solving for ΔV_{CE} and v_{in} (see Fig. 9.20):

$$\Delta V_{CE} = 10^5 (\Delta I_C - 100 \Delta I_B)$$

$$v_{in} = \Delta I_B (1258 + 100 (\Delta I_B + \Delta I_C))$$

$$0 = 60 \Delta I_C + \Delta V_{CE} + 100 (\Delta I_B + \Delta I_C)$$

Rearranging the above equations, we have

$$v_{in} = 1358 \Delta I_B + 100 \Delta I_C$$

$$0 = 100160 \Delta I_C - 999900 \Delta I_B$$

$$\Delta I_C = v_{in} / 113.58$$

The output voltage is

$$v_{out} = -\Delta I_C (60) = -60 \frac{v_{in}}{113.58} =$$

$$= -0.528 v_{in}$$

The voltage gain is

$$A_V = \frac{v_{out}}{v_{in}} = -0.528$$

(d) The input resistance is


$$r_i = \frac{v_{in}}{\Delta I_B} = 11.4 \text{ k}\Omega$$

(e) The output resistance is

$$r_o = R_C \parallel (1/h_{oe}) = 99.9 \Omega$$

9.8

The small signal circuit is shown below.

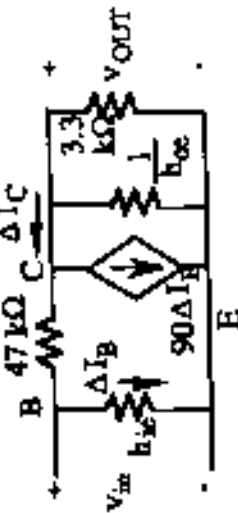

In the circuit

$$\Delta I_B = \frac{v_{in}}{h_{ie}}$$

$$\Delta I_C = - \frac{v_{out}}{3.3 \text{ k}\Omega} \left| \frac{1}{h_{oc}} \right|$$

Applying KCL at the collector, we have


$$\frac{v_{in} - v_{out}}{47 \text{ k}\Omega} = \frac{v_{out}}{2.36 \text{ k}\Omega} - 90 \frac{v_{in}}{h_{ie}}$$

Solving the above equation, we have

$$A_V = \frac{v_{out}}{v_{in}} = \frac{1/47 - 90/1.3}{1/2.36 + 1/47} = -155.5$$

9.15

(a) The AC circuit is shown below

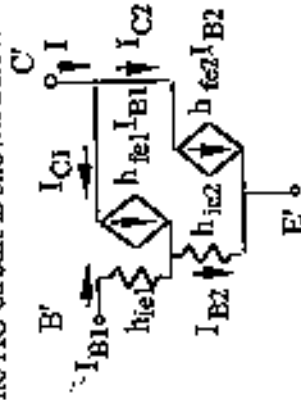

The current gain is

$$A_i = \frac{I}{I_{B1}} = \frac{I_{C1} + I_{C2}}{I_{B1}}$$

$$= \frac{I_{C1}}{I_{B1}} + \frac{I_{C2}}{I_{B1}}$$

$$= h_{fe1} + \frac{h_{fe2} I_{B2}}{I_{B1}}$$

$$= h_{fe1} + h_{fe2} \frac{I_{E1}}{I_{B1}}$$

$$= h_{fe1} + h_{fe2} (h_{fe1} + 1) \frac{I_{B1}}{I_{B1}} = 9300$$

(b) We have

$$V_{in} = I_{B1} h_{ie1} + (I_{B1} + h_{fe1} I_{B1}) h_{ie2}$$

Therefore, the input resistance is

$$R_{in} = \frac{V_{in}}{I_{B1}} = h_{ie1} + (1 + h_{fe1}) h_{ie2} = 1500 + 131 \times 200 = 27.7 \text{ k}\Omega$$