

12.23


The Karnaugh map is shown below.

CD \ AB	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	0	1	0	1
10	1	1	0	1

The map leads to the expression


$$f = \bar{B}\bar{C} + A\bar{B} + \bar{A}BC + \bar{B}\bar{D}$$

and to the gate realization shown below.

 


12.25

A	B	C	D	F
0	0	0	0	0
0	0	0	1	X
0	0	1	0	0
0	0	1	1	1
0	1	0	0	X
0	1	0	1	X
0	1	1	0	1
0	1	1	1	X
1	0	0	0	0
1	0	0	1	1
1	0	1	0	0
1	0	1	1	X
1	1	0	0	1
1	1	0	1	X
1	1	1	0	X
1	1	1	1	1

 

12.28

 


$$F = \bar{B}\bar{D} + A\bar{D} + ABC\bar{C} + \bar{A}BCD$$


12.30

$$\begin{aligned} (a) &= \bar{A}\bar{B} & (b) &= \overline{B+C} \\ f &= (a) + (b) = \bar{A}\bar{B} + \overline{B+C} \\ &= \bar{A} + \bar{B} + \bar{B}\bar{C} = \bar{A} + \bar{B} \end{aligned}$$

12.33

 

$$f(A,B,C) = ABC$$

 

$$F = B + D$$

12.36

The appropriate truth table can be constructed as follows:

A B C D	F4	F3	F2	F1	F0
0000	0	0	0	0	0
0001	0	0	0	1	0
0010	0	0	0	0	1
0011	0	0	1	1	0
0100	0	0	0	1	0
0101	0	1	0	1	0
0110	0	0	0	1	1
0111	0	1	1	1	0
1000	0	0	1	0	0
1001	1	0	0	1	0
1010	0	0	1	0	1
1011	1	0	1	1	0
1100	0	0	1	1	0
1101	1	1	0	1	0
1110	0	0	1	1	1
1111	1	1	1	1	0

Next, we construct a Karnaugh map for each bit of the output, and determine its corresponding function.

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	0	1	1
10	0	0	0	0

$F_4 = AD$

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	0	0	0

$F_3 = BC$

AB \ CD	00	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	1	1	1
10	0	0	1	1

$F_2 = AB + A\bar{D}$

AB \ CD	00	01	11	10
00	0	1	1	0
01	1	1	1	1
11	1	1	1	1
10	0	1	1	0


F_1

$$F_1 = B + D$$

		F_0			
	AB	00	01	11	10
CD	00	0	0	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1

$$F_0 = C\bar{D}$$

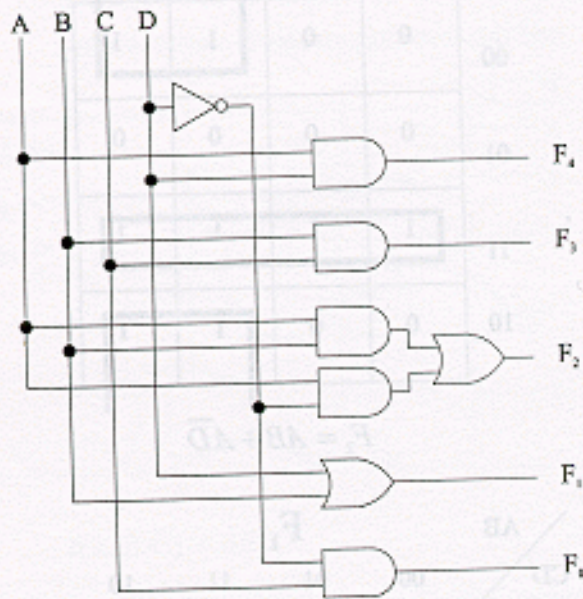The corresponding circuits are shown below:



This completes the design.

12.46

Assuming that the enable input (EN) is active high, when EN is logic 0 (A is logic 1), all decoder outputs of the first decoder are forced to logic 1 independent of the inputs. However, when EN is logic 1 (A is logic 0), all decoder outputs of the second decoder are forced to logic 1 independent of the select inputs. Therefore, A functions as the fourth bit of the select inputs. Thus, the circuit operates as a 4 of 16 decoder.

12.49

$$f = \bar{A}B\bar{C} + A\bar{B}C + AC$$

	A	0	1
BC	00	0	1
	01	0	1
	11	0	1
	10	1	0

From the truth table it is clear that:

$$I_0 = 0$$

$$I_1 = \bar{C}$$

$$I_2 = 1$$

and

$$I_3 = C$$