
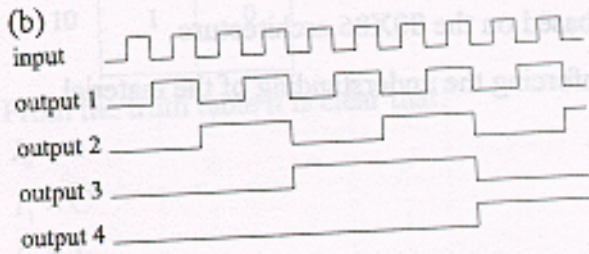


13.1

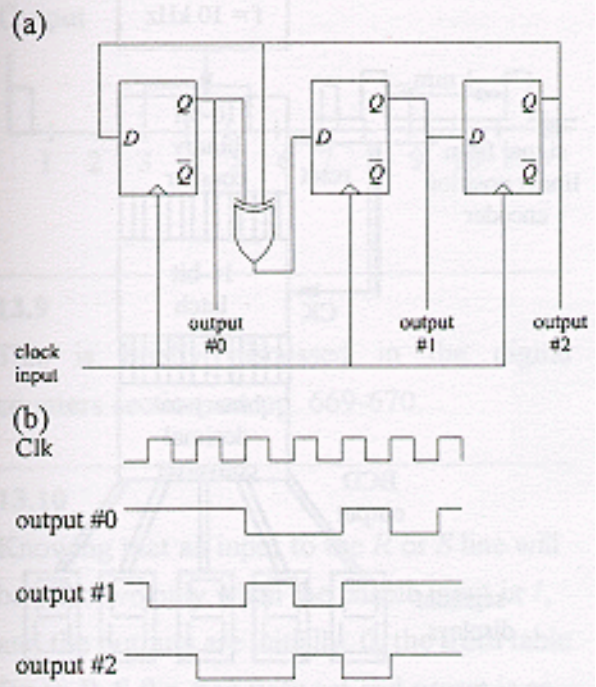(a) The device is called a MOD-16 ripple counter. It can count clock pulses from 0 to (2^4-1) . The outputs divide the frequency by 2^1 , 2^2 , 2^3 , and 2^4 respectively. Therefore, you can use this circuit as a divide by N counter, where N is 2, 4, 8 and 16.




13.4



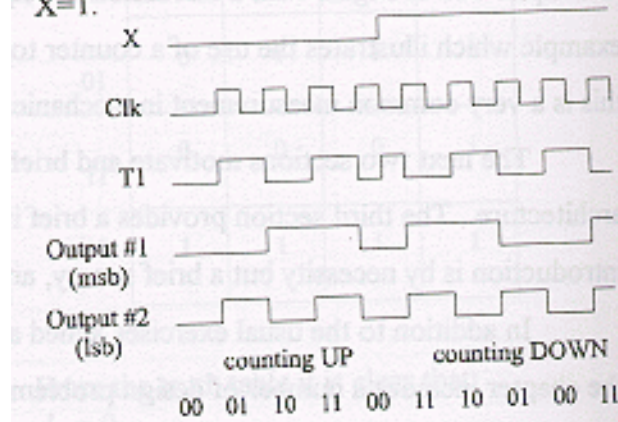
13.3

The basic operation of the circuit is to count up when $X=0$, and to count down when $X=1$.



Clock	X	Output #2	T ₁	Output #1
↑	0	0	0	No change
↑	1	1	0	No change
↑	0	1	1	toggle
↑	1	0	1	toggle

13.8

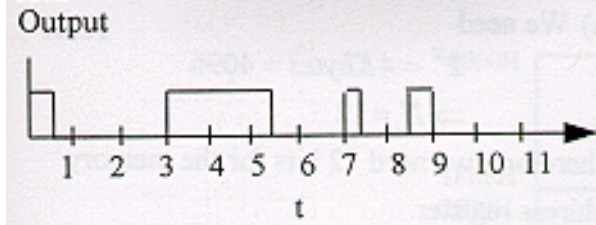

13.17

$$640K \text{ bytes} = 640 \times 1024 = 655,360 \text{ bytes}$$

$$(a) \ 655360 \times \frac{1 \text{ word}}{2 \text{ bytes}} = 327680 \text{ words}$$

$$(b) \ 655360 \text{ bytes} \times \frac{2 \text{ nibbles}}{1 \text{ byte}} = 1310720 \text{ nibbles}$$

$$(c) \ 655360 \text{ bytes} \times \frac{8 \text{ bits}}{1 \text{ byte}} = 5242880 \text{ bits}$$

$$(d) \ 1 \text{ Mbyte} = 1024 \text{ Kbytes}$$

$$\therefore \text{ we need } 1024 - 640 = 384 \text{ Kbytes}$$

$$\text{or } 384 \times 8 = 3072 \text{ Kbits}$$

$$\text{or } \frac{3072}{256} = 12 \text{ of the 256Kbit chips.}$$

$$\text{Cost} = 12 \times \$0.20 = \$2.40$$

13.18

$$a) \ n(n-1)$$

$$b) \ 2n$$

13.19

(a) We need

$$2^N = 4 \text{ Kbytes} = 4096$$

$$\Rightarrow N = 12$$

Therefore, we need 12 bits for the memory address register.

(b) The data register must be at least as large as each word in memory. Therefore, the data register must be 16 bits in length.

13.22

$$\frac{8 \text{ tracks}}{\text{cm}} \times 2 \text{ cm} = 16 \text{ tracks}$$

$$16 \text{ tracks} \times 200 \frac{\text{bits}}{\text{cm}} = 3200 \frac{\text{bits}}{\text{cm}}$$

$$3200 \frac{\text{bits}}{\text{cm}} \times \frac{1 \text{ byte}}{8 \text{ bits}} = 400 \frac{\text{bytes}}{\text{cm}}$$

$$400 \frac{\text{bytes}}{\text{cm}} \times 25 \frac{\text{cm}}{\text{s}} = 10000 \frac{\text{bytes}}{\text{s}}$$