

14.5

(a) $V_{out} = i_D R_L$

Given a large enough value of V_D , $V_{out} = 0.5 \times 10^{-6} H R_L$; hence, varies linearly with H .

(b) $1 = 0.5 \times 10^{-6} (1500) R_L$

$R_L = 1333\Omega$

14.8

$$\text{mean} = \frac{\sum \text{measurements}}{20} = 9.945 \pm 2\%$$

max. = 10.144

min. = 9.746

$$\text{average deviation} = \frac{\sum |\text{deviations}|}{20} = 0.225$$

$$\text{standard deviation} = \sqrt{\frac{\sum |\text{deviations}|^2}{20}} = 0.427$$

Measurement #1 exceeds the standard deviation \Rightarrow probability $< 0.99 \Rightarrow$ roller speed will be adjusted

14.10

(a) (b) and (c) are precise, (a) and (d) are not.

(b) (a) and (c) are accurate, (b) and (d) are not.

14.11

$$A = 1 + \frac{2R_2}{R_1} = 1 + \frac{1(5k\Omega)}{1k\Omega} = 1 + 10 = 11$$

14.17

$$CMRR_{dB} = 20 \log_{10} \left| \frac{A_{diff}}{\frac{R_F}{R} \left(\frac{R + R_F}{R_F + R + \Delta R} - 1 \right) A} \right|$$

$$A_{diff} = A \times \frac{R_F}{R}$$

$$\Delta R = 0.02 \times R = 0.02 \times 1k\Omega = 20\Omega$$

$$CMRR_{dB} = 20 \log_{10} \left| \frac{A \frac{R_F}{R}}{\frac{R_F}{R} \left(\frac{R + R_F}{R_F + R + \Delta R} - 1 \right) A} \right|$$

$$= 20 \log_{10} \left| \frac{1}{\frac{R + R_F}{R_F + R + \Delta R} - 1} \right|$$

$$= 20 \log_{10} \left| \frac{1}{\frac{1000 + 200000}{200000 + 1000 + 20} - 1} \right|$$

$$\approx 80dB$$

14.32

$$f_c = 10 \text{ Hz} = \frac{1}{2\pi RC}$$

$$\Rightarrow \omega_c = \frac{1}{RC} = 2\pi \times 10 = 20\pi \frac{\text{rad}}{\text{s}}$$


Choose $R = 20k\Omega$. Then,

$$\frac{1}{(20k\Omega)C} = 20\pi \Rightarrow C = \frac{1}{20 \times 10^3 \times 20\pi} = 796nF$$

and the two capacitors have values given by

$$\sqrt{2}C = 1.125\mu F \text{ and } \frac{C}{\sqrt{2}} = 563nF.$$

14.34

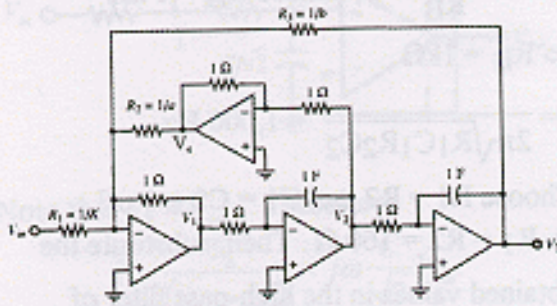

Using Laplace transforms, note that

$$V_2 = -\frac{1}{s}V_1$$

$$V_3 = -\frac{1}{s}V_2 = \frac{1}{s^2}V_1$$

and

$$V_4 = -V_2 = \frac{1}{s}V_1$$

Writing a KCL equation at the inverting input to the leftmost op-amp,

$$-KV_{in} - V_1 - aV_4 - bV_3 = 0$$

or

$$-KV_{in} - V_1 - \frac{a}{s}V_1 - \frac{b}{s^2}V_1 = 0$$

$$\Rightarrow \frac{V_1}{V_{in}} = -\frac{Ks^2}{s^2 + as + b}$$

which is a second-order high-pass function.

Also,

$$\frac{V_2}{V_{in}} = -\frac{1}{s} \frac{V_1}{V_{in}} = \frac{Ks}{s^2 + as + b}$$


which is a bandpass function, and

$$\frac{V_3}{V_{in}} = \frac{1}{s^2} \frac{V_1}{V_{in}} = -\frac{K}{s^2 + as + b}$$

which is a low-pass function.

14.36

The circuit is shown below:

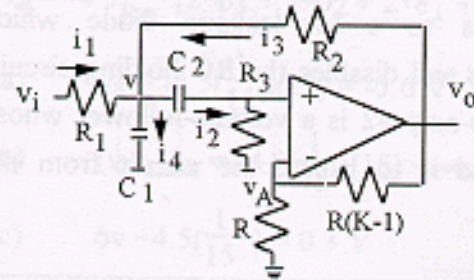

We have

$$v_A = \frac{R v_o}{R + R(K-1)} = \frac{v_o}{K}$$

$$i_1 = \frac{v_i - v}{R_1}$$

$$i_2 = \frac{v - v_A}{1/j\omega C_2} = \frac{v_A}{R_3}$$

$$i_3 = \frac{v_o - v}{R_2}$$

$$i_4 = \frac{v}{1/j\omega C_1}$$

From $i_2 = \frac{v_A}{R_3} = \frac{v - v_A}{1/j\omega C_2}$, we have

$$v = \frac{v_A}{j\omega C_2 R_3} + v_A = \left(\frac{1}{j\omega C_2 R_3} + 1\right) \frac{v_o}{K}$$

From $i_1 + i_3 = i_2 + i_4$, we have

$$\begin{aligned} & \frac{v_i}{R_1} - \left(\frac{1}{j\omega C_2 R_3} + 1\right) \frac{v_o}{KR_1} \\ & + \frac{v_o}{R_2} - \left(\frac{1}{j\omega C_2 R_3} + 1\right) \frac{v_o}{KR_2} \\ & = \frac{v_o}{KR_3} + \left(\frac{j\omega C_1}{j\omega C_2 R_3} + j\omega C_1\right) \frac{v_o}{K} \end{aligned}$$

The frequency response therefore is:

$$\frac{v_o(j\omega)}{v_i(j\omega)} = \frac{j\omega K/C_1 R_1}{(j\omega)^2 + K_1 j\omega + K_2}$$

where

$$K_1 = \frac{1}{C_1 R_1} + \frac{1}{C_2 R_3} + \frac{1}{R_1 C_1} - \frac{K}{R_2 C_1} + \frac{1}{R_2 C_1}$$

and

$$K_2 = \frac{R_1 + R_2}{R_1 R_2 R_3 C_1 C_2}$$