

14.42

$$v_a = -4.5 \frac{R_f}{R_0} [2^3 b_3 + 2^2 b_2 + 2^1 b_1 + b_0]$$

$$a) \quad v_a = -4.5 \left(\frac{1}{15}\right)(12) = -3.6 \text{ V}$$

$$b) \quad (v_a)_{\max} = -4.5 \left(\frac{1}{15}\right)(15) = -4.5 \text{ V}$$

$$c) \quad \delta v = 4.5 \left(\frac{1}{15}\right) = 0.3 \text{ V}$$

$$d) \quad n \geq \frac{\log\left(\frac{|(v_a)_{\max} - (v_a)_{\min}|}{\delta v} + 1\right)}{\log 2}$$

$$\text{or} \quad n \geq 7.82$$

Therefore, we choose $n = 8$.

14.46

For the circuit of Figure P14.13, $R_0 = 1 \text{ k}\Omega$
and $n = 4$.

$$\text{Therefore,} \quad (v_a)_{\max} = -10 \text{ V}$$

$$\text{and} \quad -10 = -5 \frac{R_f}{1000}(15)$$

$$\text{or} \quad R_f = 133.3 \Omega$$

14.44

This circuit is just a summing amplifier, with

$$v_o = -\frac{R_2}{R_1} b_3 V - \frac{R_2}{2R_1} b_2 V - \frac{R_2}{4R_1} b_1 V - \frac{R_2}{8R_1} b_0 V$$

$$= -\frac{R_2 V}{R_1} \left(b_3 + \frac{b_2}{2} + \frac{b_1}{4} + \frac{b_0}{8} \right)$$

$$= -\frac{R_2 V}{8R_1} (8b_3 + 4b_2 + 2b_1 + b_0)$$

14.49

$$a) \quad v_a = -10 \left(\frac{1}{4095}\right)(345) = -0.8425 \text{ V}$$

$$b) \quad (v_a)_{\max} = -10 \left(\frac{1}{4095}\right)(4095) = -10 \text{ V}$$

$$c) \quad \delta v = 10 \left(\frac{1}{4095}\right) = 2.44 \text{ mV}$$

$$d) \quad n \geq \frac{\log\left(\frac{|(v_a)_{\max} - (v_a)_{\min}|}{\delta v} + 1\right)}{\log 2}$$

$$\text{or} \quad n \geq 14.288$$

Therefore, we choose a 15-bit ADC.

14.52

$$n \geq \frac{\log\left(\frac{30}{0.01} + 1\right)}{\log 2} = 11.55$$

Choose $n = 12$.

14.56

$$(a) \quad \text{resolution} = 2^{-3} \times 10V = 1.25V$$

$$(b) \quad \text{resolution} = 2^{-8} \times 10V = 39.0625mV$$

$$(c) \quad \text{more bits} \Rightarrow \text{better resolution}$$

14.64

$$(a) \quad 5\% \Rightarrow 2^{-n} \leq 0.05 \Rightarrow n = 5$$

$$(b) \quad 2\% \Rightarrow 2^{-n} \leq 0.02 \Rightarrow n = 6$$

$$(c) \quad 1\% \Rightarrow 2^{-n} \leq 0.01 \Rightarrow n = 7$$

14.70

(a) Define $V_2 = \frac{R_1}{R_2 + R_1}V$ as the voltage at the inverting input of the op-amp. Then:

When $V_{in} > V_2$ the output of the op-amp will be positive and the green LED will turn on (*go*).

When $V_{in} < V_2$ the output of the op-amp will be negative and the red LED will turn on (*no go*).

(b) For this design, $V_2 = 5V$ and $V = 15V$.

$$\therefore \frac{R_1}{R_2 + R_1} 15V = 5V$$

$$\Rightarrow \frac{R_1}{R_2 + R_1} = \frac{1}{3}$$

or $\frac{R_2}{R_1} + 1 = 3$

$$\Rightarrow \frac{R_2}{R_1} = 2$$

Choose $R_1 = 10k\Omega$ and $R_2 = 20k\Omega$ to complete the design