

**8.125** Calculate the Thévenin equivalent impedance  $Z_{Th}$  in the circuit shown in Fig. P8.125.


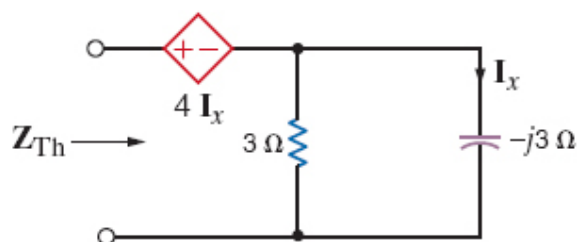


Figure P8.125

**SOLUTION:**

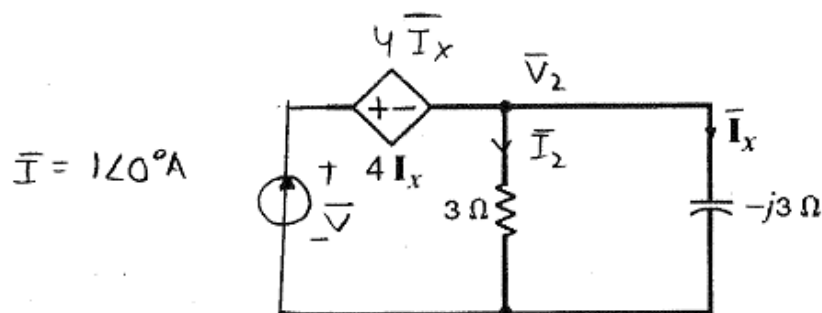

$$\text{KCL at } \textcircled{2} : 1\angle 0^\circ = I_2 + I_x$$

$$\frac{\bar{V}_2}{3} + \frac{\bar{V}_2}{-j3} = 1\angle 0^\circ$$

$$-j1\bar{V}_2 + \bar{V}_2 = -j3(1\angle 0^\circ)$$

$$\bar{V}_2(1-j1) = 3\angle -90^\circ$$

$$\bar{V}_2 = 2.12\angle -45^\circ \text{ V}$$

$$I_2 = \frac{\bar{V}_2}{3} = \frac{2.12\angle -45^\circ}{3} = 0.707\angle -45^\circ \text{ A}$$

$$I_x = \frac{\bar{V}_2}{-j3} = \frac{2.12\angle -45^\circ}{-j3} = 0.707\angle 45^\circ \text{ A}$$

$$\text{KVL: } \bar{V} = 4\bar{I}_x + 3\bar{I}_2$$

$$\bar{V} = 4(0.707 \angle 45^\circ) + 3(7.07 \angle -45^\circ)$$

$$\bar{V} = 3.54 \angle 8.13^\circ \text{ V}$$

$$\bar{Z}_{TH} = \frac{\bar{V}}{\bar{I}} = \frac{3.54 \angle 8.13^\circ}{1 \angle 0^\circ}$$

$$\bar{Z}_{TH} = 3.54 \angle 8.13^\circ \Omega$$

**9.57** The current waveform in Fig. P9.57 is flowing through a  $5\text{-}\Omega$  resistor. Find the average power absorbed by the resistor.

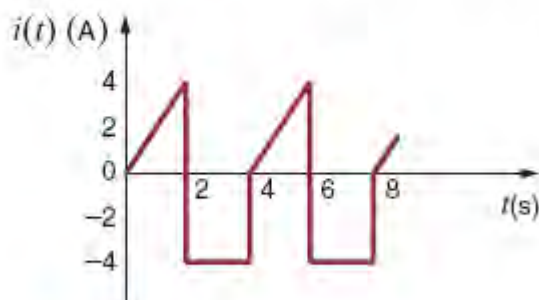


Figure P9.57

**SOLUTION:**

$$i_1(t) = 2t$$

$$i_1^2(t) = 4t^2$$

$$i_2(t) = -4$$

$$i_2^2(t) = 16$$

$$\int_0^2 i_1^2(t) dt = \int_0^2 4t^2 dt = \frac{4t^3}{3} \Big|_0^2 = \frac{32}{3}$$

$$\int_2^4 i_2^2(t) dt = \int_2^4 16 dt = 16t \Big|_2^4 = 32$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

$$I_{rms} = \sqrt{\frac{1}{4} \left[ \frac{32}{3} + 32 \right]}$$

$$I_{rms} = 3.27 \text{ A}$$

$$P_{5\Omega} = I_{rms}^2 R$$

$$P_{5\Omega} = (3.27)^2 (5)$$

$$P_{5\Omega} = 53.46 \text{ W}$$

- 14.64** Determine the transfer function for the network shown in Fig. P14.64. If a step function is applied to the network, what type of damping will the network exhibit?


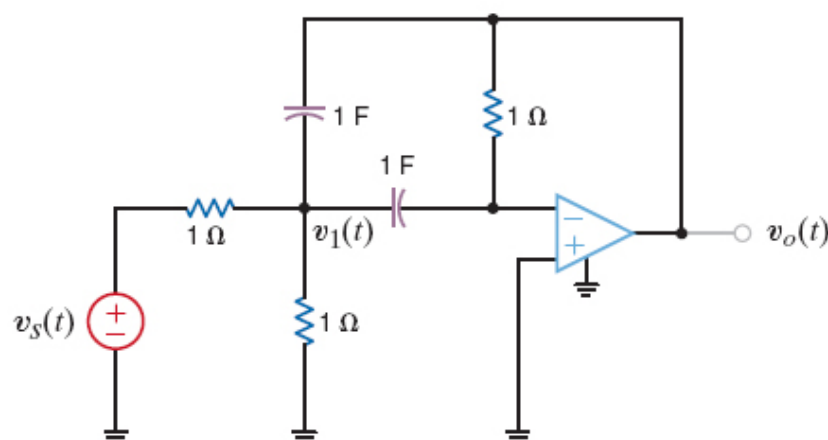


Figure P14.64

**SOLUTION:**

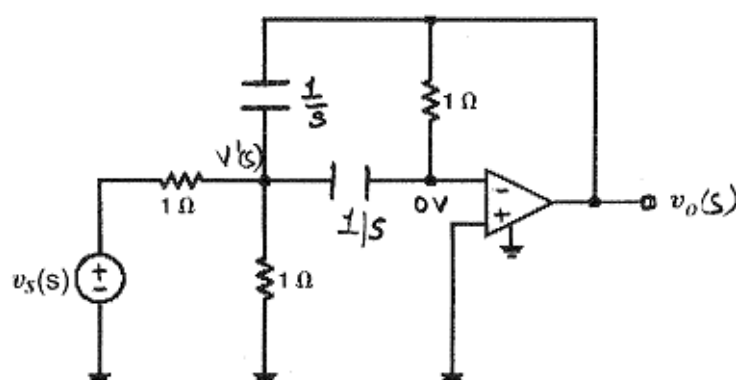

$$\frac{V_s(s) - V_1(s)}{1} = \frac{V_1(s)}{1} + V_1(s)S + (V_1(s) - V_o(s))S$$

$$\frac{V_o(s)}{1} + V_1(s)S = 0$$

$$V_1(s) = -\frac{V_o(s)}{S}$$

$$V_s(s) = (2S + 2)V_1(s) - S V_o(s)$$

$$V_s(s) = -\left(\frac{S^2 + 2S + 2}{S}\right)V_o(s)$$

$$\frac{V_o(s)}{V_s(s)} = \frac{-S}{S^2 + 2S + 2}$$

The roots are:

$$s = \frac{-2 \pm \sqrt{2^2 - 4(1)(2)}}{2(1)} = -1 \pm j1$$

Complex conjugate poles. Therefore, the network is underdamped.

**16.15** Find the Z parameters of the two-port network in Fig. P16.15.


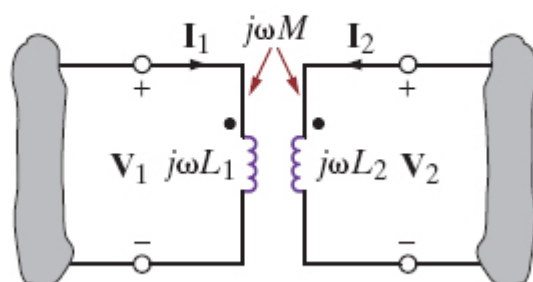


Figure P16.15

**SOLUTION:**

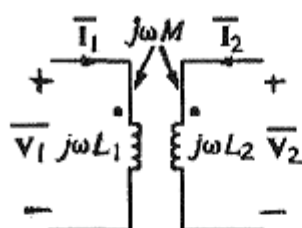

$$\bar{V}_1 = \bar{I}_1 (j\omega L_1) + \bar{I}_2 (j\omega M)$$

$$\bar{V}_2 = \bar{I}_1 (j\omega M) + \bar{I}_2 (j\omega L_2)$$

$$\bar{Z}_{11} = j\omega L_1$$

$$\bar{Z}_{12} = j\omega M$$

$$\bar{Z}_{21} = j\omega M$$

$$\bar{Z}_{22} = j\omega L_2$$

**15.29** Determine the steady-state voltage  $v_o(t)$  in the network in Fig. P15.29a if the input current is given in Fig. P15.29b.

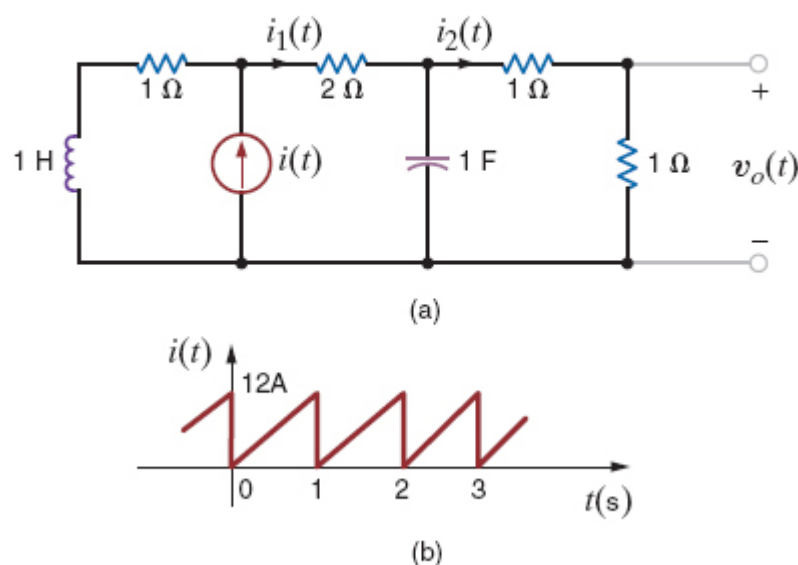


Figure P15.29


**SOLUTION:**

$$T_0 = 1 \text{ s} \quad \text{and} \quad \omega_0 = 2\pi \text{ rad/s}$$

$i(t)$  can be found from Table 15.2:

$$i(t) = 6 + \sum_{n=1}^{\infty} \frac{-12}{n\pi} \sin 2n\pi t \quad \text{A}$$

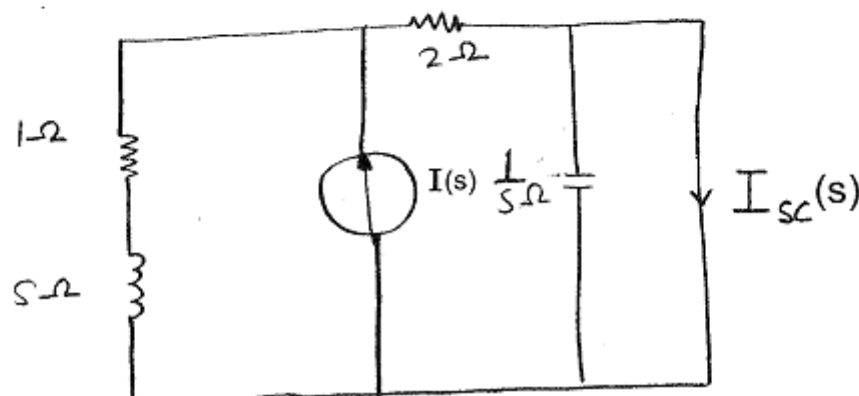
$$i(t) = 6 + \sum_{n=1}^{\infty} \frac{-12}{n\pi} \cos(2\pi nt - 90^\circ) \quad \text{A}$$



$$I_{sc}(s) = \left( \frac{s+1}{s+3} \right) \bar{I}$$

$$Z_{TH}(s) = \frac{\frac{1}{s}(s+3)}{s+3 + \frac{1}{s}}$$

$$Z_{TH}(s) = \frac{s+3}{s^2+3s+1}$$

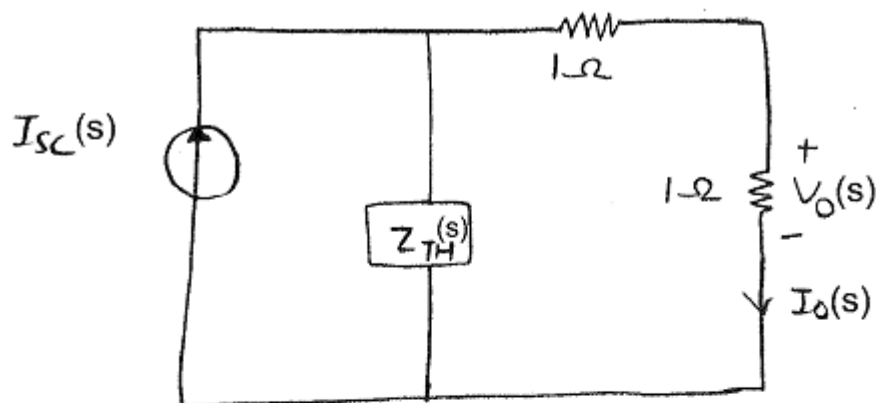

$$V_o(s) = 1 I_o(s)$$

$$\frac{I_o(s)}{I_{sc}(s)} = \frac{Z_{TH}(s)}{2 + Z_{TH}(s)}$$

$$\frac{V_o(s)}{I_{sc}(s)} = \frac{s+3}{s+3+2s^2+6s+2}$$

$$\frac{V_o(s)}{I_{sc}(s)} = \frac{s+3}{(2s+5)(s+1)}$$

$$\frac{V_o(s)}{I(s)} = \frac{s+3}{(2s+5)(s+1)} \left( \frac{s+1}{s+3} \right)$$



$$\frac{V_o(s)}{I(s)} = \frac{1}{2s+5}$$

$$s = j2\pi n$$

$$\frac{\bar{V}_o}{\bar{I}} = \frac{1}{5+j4\pi n}$$

let

$$A(n) = \frac{1}{5+j4\pi n}$$

$$A(n) = |A(n)| \angle \theta_{A(n)}$$

$$n=0, i(t) = 6A \text{ and } A(0) = 1/5$$

$$V_o(t) = \frac{6}{5} + \sum_{n=1}^{\infty} \frac{-12}{n\pi} |A(n)| \cos(2\pi n t - 90^\circ + \theta_{A(n)}) V$$